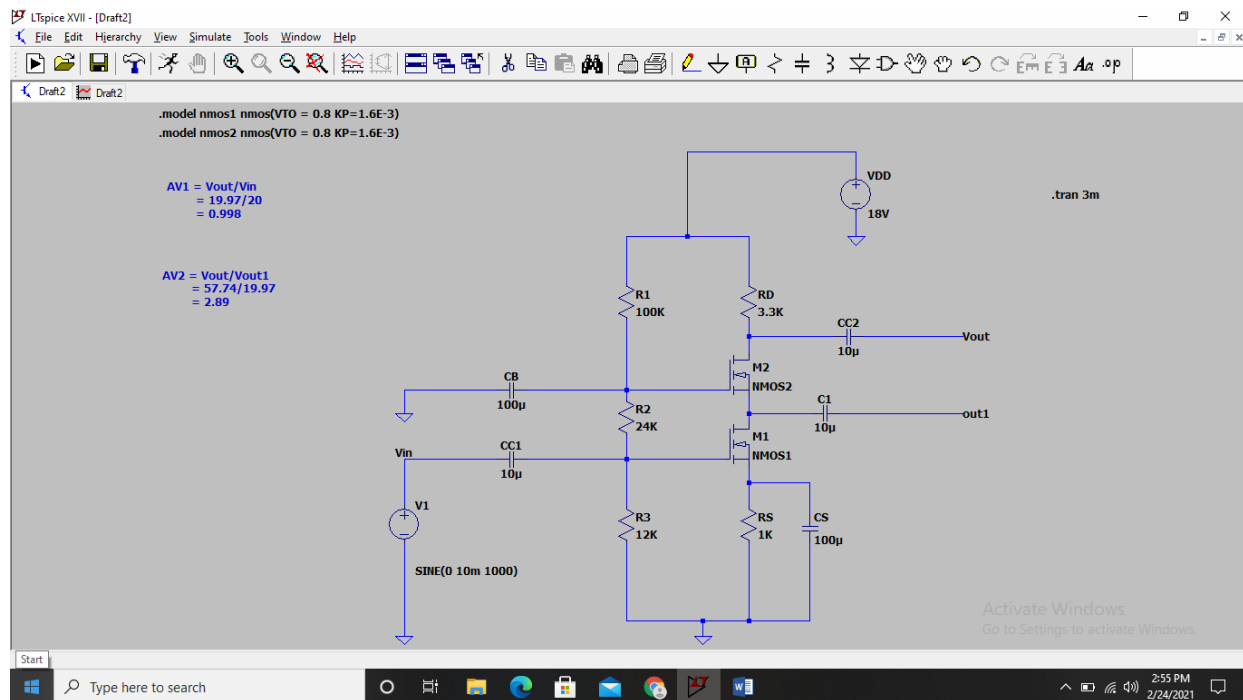


EXPERIMENT NO. 2

AIM: To determine voltage gain of CS-CG MOSFET Cascode amplifier using LTspice

Software Required: Ltspice


Circuit diagram:



Introduction:

An important amplifier configuration is known as cascode amplifier. It consists of a common-source (CS) stage followed by a common-gate (CG) stage as shown in figure. The common-source configuration presents a relatively high input resistance to the signal source.

The common-gate configuration presents a very low input resistance. By replacing the drain resistance R_D in the CS amplifier stage with a common gate CG amplifier stage, the CS-CG configuration virtually eliminates the Miller effect. This will lead to higher 3dB frequency than is possible with a simple common-source amplifier. An extension in the upper cutoff frequency is achieved without reducing the midband gain, since the drain of Q_2 carries a current almost equal to the drain current of Q_1 . Another reason for extending the upper cutoff frequency is that, in the CG configuration the Miller effect does not exist and does not limit the high-frequency response. Notice that the effective load resistance seen by the CS transistor Q_1 is very low and equal to the input resistance of the CG transistor Q_2 . The transistor Q_2 acts as a current buffer or an impedance transformer.

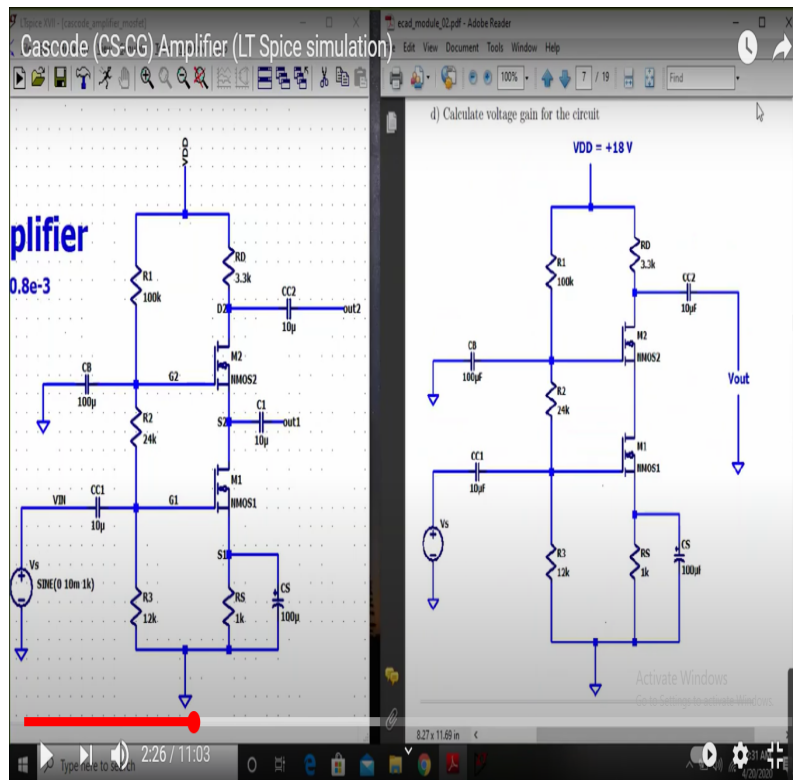

Experiment Procedure:

- 1) Open New Schematics, Use the components icon to enter the components menu and select a component/device. Place the component/device on your schematics
- 2) Place all the required component/device on your schematics, assign value and names by double click. Click on wire icon to connect the components.
- 3) Set input as AC signal with 10mV at 1KHz. Also click on Edit- Text- Spice directory and set NMOS parameters.
- 4) Now go to Edit Simulation cmd and select transient of 3ms
- 5) Save the schematics in the desired folder and click on Run icon to stimulate the circuit.
- 6) A new output window will pop out. Add plots and trace input voltage Vin, output voltage of stage 1 Vout1 and output voltage of stage 2 Vout.
- 7) Now left click twice on Vout1 and Vout to note the peak to peak voltage.

OBSERVATION:

The output of stage 1 i.e. Vout 1 is out of phase with input and has gain approximately equal to 1. The output of stage 2 is in phase with its input and overall gain is gain of stage 2.

CALCULATIONS:

$$AV1 = V_{out}/V_{in}$$

$$= 19.97/20$$

$$= 0.998$$

$$AV2 = V_{out}/V_{out1}$$

$$= 57.74/19.97$$

$$= 2.89$$

$$AV = AV1 \times AV2$$


$$= 2.88$$

CONCLUSION:

The voltage gain of first stage i.e. of CS is unity and the actual gain of the cascode amplifier is provided by second stage i.e. CG stage.

Result:

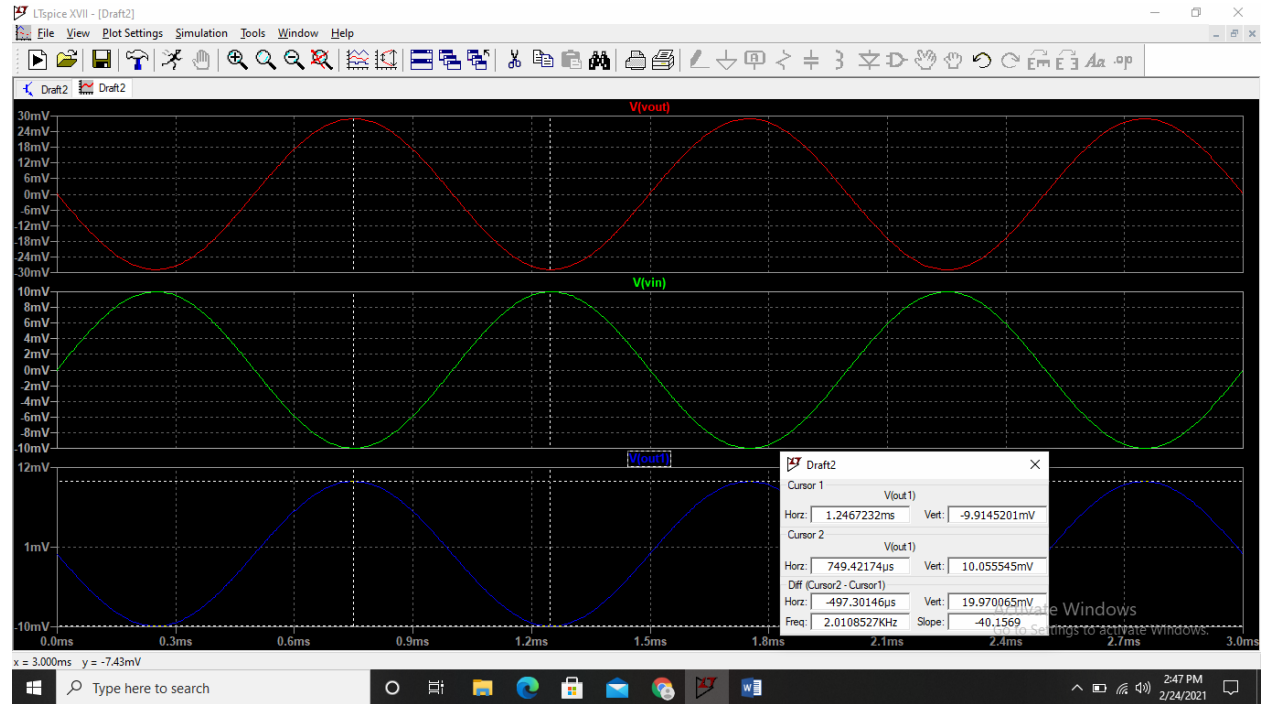Finding amplitude of output of stage 1(V_{out1}) to calculate AV_1



Finding amplitude of output of stage 2(V_{out}) to calculate AV_2

